


**S.V. National Institute of Technology, Surat**  
B.Tech (II) CO, 3<sup>RD</sup> Sem      Endsem Exam  
EC207: DIGITAL CIRCUITS

Dec. 2014

Time: 3Hr.]

[Total Marks: 100

 - Q.1 (a)** Perform following operation without converting numbers to any other base. [4]  
(1)  $(345)_7 + (603)_7$       (2)  $(538)_{13} - (203)_{13}$
- (b)** (i) Obtain 8x1 multiplexer using 2x1 multiplexers and inverters. [6]  
(ii) Realize 4x16 decoder using only 1x2 decoders (having enable input).
- (c)** Draw octal to binary priority encoder. Include an output V to indicate that at least one input is 1. [4]
- (d)** Design logic circuit that generates 9's complement of input BCD digit. [4]
- (e)** Simplify following functions using tabulation (Quine-McCluskey) method. [8]  
 $F(A,B,C,D,E) = \sum m(6,9,13,18,19,25,27)$
- Q.2 (a)** Design a BCD to Excess-3 code converter using minimum number of NAND gates [4]
- (b)** Design and sketch single bit full adder/subtractor circuit with one additional control input M such that when M=0 it acts as full adder and when M=1 it acts as full subtractor. [6]
- (c)** Implement the following function using (i) 8x1 Mux (ii) 4x1 Mux [6]  
 $f(w,x,y,z) = wx' + w'xz' + x'y'z + x'yz$
- (d)** Derive the PLA programming table for the combinational circuit that multiplies two 2-bit input binary numbers. Minimize the number of product terms. [8]
- Q.3 (a)** Draw the logic circuit *mod-13 ripple* counter using positive edge triggered T flip-flops. [4]
- (b)** Implement 4-bit shift register using D flip-flops and multiplexers that uses 2-bit control signal  $S_1S_0$ . Realize four register operations: 00 (parallel load), 01 (shift left), 10 (shift right) and 11 (no change) [4]
- (c)** Draw logic circuit of 3-bit synchronous parallel counter using JK flip-flops. Write expression of minimum clock period? Draw waveforms of clock and output of each flip-flop for 6 clock cycles. [6]
- (d)** Design and implement sequence generator that generate sequence **10011010** and repeat. [8]
- (e)** Obtain state table and draw state diagram for following logic circuit. Initial state of the circuit is **00**. [6]



- Q.4 (a)** Design synchronous counter that generates sequence 1,7,2,5,3 and repeat. Make sure that counter is automatically reset when any unused state occurs. [8]
- (b)** Draw the logic circuit of edge triggered D flip-flop that uses *three basic flip-flops* and explain its operation. What do you mean by setup time and hold time? [6]
- (c)** A 24-bit floating-point *binary* number has 9 bits for exponent and 15 bits for coefficient. The coefficient is assumed to be a normalized fraction. The binary numbers in coefficient and exponent are in sing-magnitude form. (i) What are the largest and smallest positive quantities that can be accommodated, excluding zero? (ii) Represent quantities  $(+23.25)_{10}$  and  $(-67.125)_{10}$  using this presentation. [4]

**OR**

Perform following arithmetic operations using 8-bit signed binary numbers represented in 2's complement form. Write binary value of carry into and out of sign-bit position, overflow bit and sign bit (8<sup>th</sup> bit) of result in each case.

(i)  $(+68)_{10} + (+76)_{10}$                       (ii)  $(+68)_{10} + (-76)_{10}$

- (d) Using 4-bit registers with parallel load capability, a quadruple 4x1 multiplexer and logic gates, draw the logic diagram to implement following RTL statements. [4]

$T_0: R1 \leftarrow R2, \quad T_1: R1 \leftarrow \overline{R2}, \quad T_2: R1 \leftarrow 0000, \quad T_3: R1 \leftarrow R1 \wedge R2$